

## chapter 1: Analysis of clocked sequential circuits

\* Some flip-flops have asynchronous i/p that are used to force the flip-flop to a particular state independently of the clock.

\* The i/p that sets the flip-flop to 1 is called preset or direct set. The input that clears the flip-flop to 0 is called clear or direct reset.

\* When power is turned on in a digital system, the state of the flip-flop is unknown. The direct i/p are useful for bringing all flip-flops in the system to known starting state prior to the clocked ops.

\* The info available in a state table can be represented graphically in the form of state diagram. In this type of diagram a state is represented by a circle & the clock-triggered transition b/w states are indicated by directed lines connecting the circles.

\* The time sequence of i/p, o/p & flip-flop states can be enumerated in a state table (transition table). The table has 4 parts: present state, next state, i/p & o/p.

\* In general a sequential ckt with 'm' flip-flops & 'n' i/p needs  $2^{m+n}$  rows in the state table.

## chapter - 2: Analysis with D-flip-flop.

\* The i/p eqn of D-flip flop is given by  $D_A = A \oplus x \oplus y$ .  $D_A$  means a D flip-flop with o/p A.

\* The x & y variables are the i/p to the eqn. No o/p eqn are given which implies that the o/p comes from the o/p of the flip-flop.

\* The state table has one column for the present state of flip-flop 'A' two columns for the two i/p, & one column for the next state of A.

\* The next-state values are obtained from the state eqn  $A(t+1) = A \oplus x \oplus y$ .

\* The eqn specifies an odd func & is equal to 1 when one variable is 1 or when all 3 variables are 1.

## Python:

### chapter 1: object oriented programming.

- ① object oriented pgm explained
- ② turning this app into oop style  
turning this app into oop style part 2
- ③ creating a bank account object
- ④ Inheritance
- ⑤ oop glossary
- ⑥ GUI in oop design (practice)
- ⑦ solution.