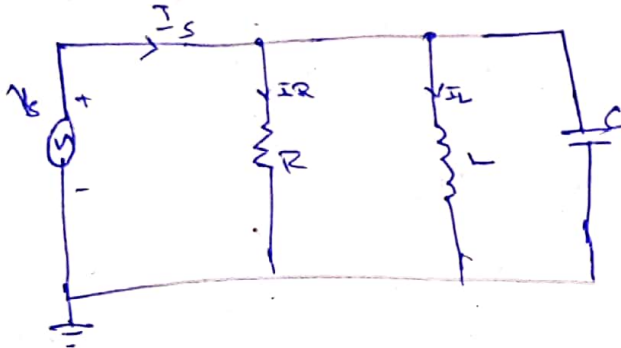



Parallel RLC & Series RLC circuit:

shashank
4A18EC048

Parallel RLC CKT:



Series RLC CKT:

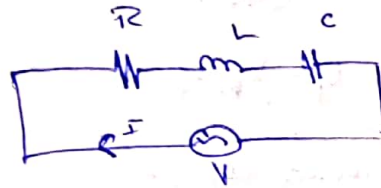


network theory:


→ Formation of tie-set & cut-set matrix & its appln in KVL & KCL

→ online open source CKT simulation - series RLC, parallel RLC, RL & RC series CKT frequency response.

→ Inductive Reactance against frequency

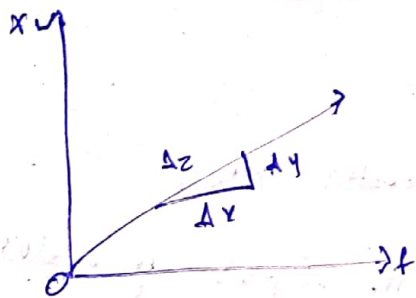

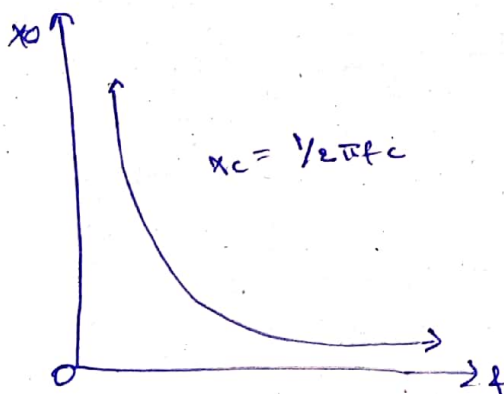→ capacitive reactance against frequency.



→ conductance, admittance & the susceptance.

* Admittance (Y) :-

$$Y = 1/Z (S)$$

* conductance (G) :-

$$G = 1/R (S)$$

* susceptance (B) :-

$$B_L = 1/X_L (S)$$

$$B_C = 1/X_C (S)$$

Series ckt :-

Voltage (V)
Resistance R
Reactance (X)
Impedance (Z)

parallel ckt

current (I)
conductance (G)
susceptance (S)
Admittance (Y)

* note Interference of the impedance of the ckt for
the → change in frequency.
→ change in parametered value (R, L, C)

python

project excellence on building geocodes web.

→ student project - how the o/p in super geocodes.

→ Auto super geocodes part 1

→ solution part 2